

# Connecting the Relay to the Galileo

## What you will need:

- Grove relay
- Grove universal 4pin cable
- Jump wires
- Intel Galileo
- Ethernet Connection
- SD Card
- Wyliodrin Account



2. Connect the live wires by inserting them into the relay and securing them with the screws.



4. Place the relay in a wiring junction box and close for safety reasons as the wires are exposed.



1. Cut the lamp wires and separate the wires inside (the live and the neutral wires)



3. Connect the neutral wires with a simple conductor.



5. Plug the Lamp into a socket.